
 


**Part A:  $W_p=W_n=1\text{ }\mu\text{m}$  ,  $L_n=L_p=0.2\text{ }\mu\text{m}$**
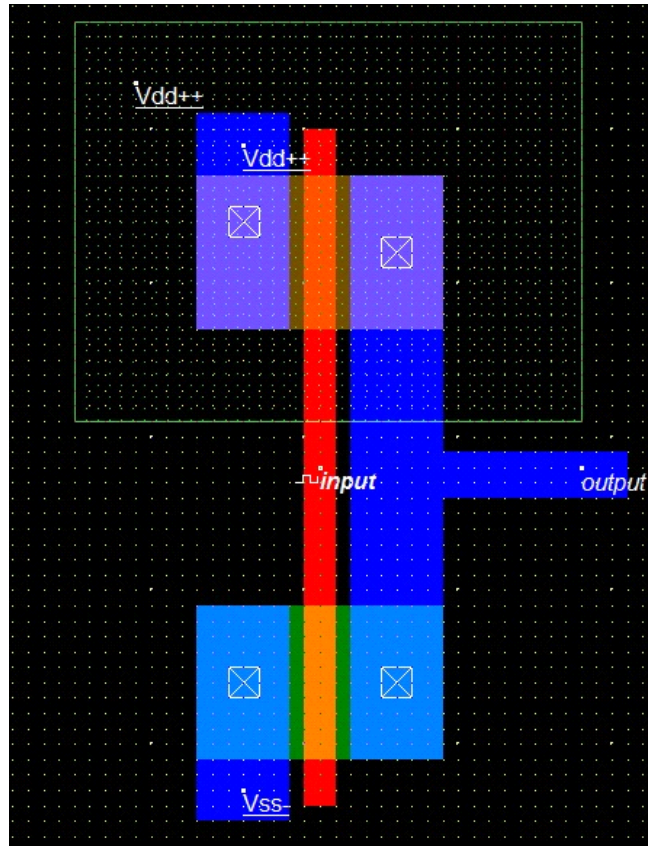
## **Design Layout & Timing Diagram of CMOS Inverter**





NAME OF THE STUDENT:

CLASS:

ROLL NUMBER:

**Part B:  $W_p=2.5W_n$  ( $W_n=1\text{ }\mu\text{m}$ ) ,  $L_n=L_p=0.2\text{ }\mu\text{m}$**
  
## **Design Layout & Timing Diagram of CMOS Inverter**





NAME OF THE STUDENT:

CLASS:

ROLL NUMBER:

**Part C:  $W_p=5W_n$  ( $W_n=1\text{ }\mu\text{m}$ ) ,  $L_n=L_p=0.2\text{ }\mu\text{m}$**
 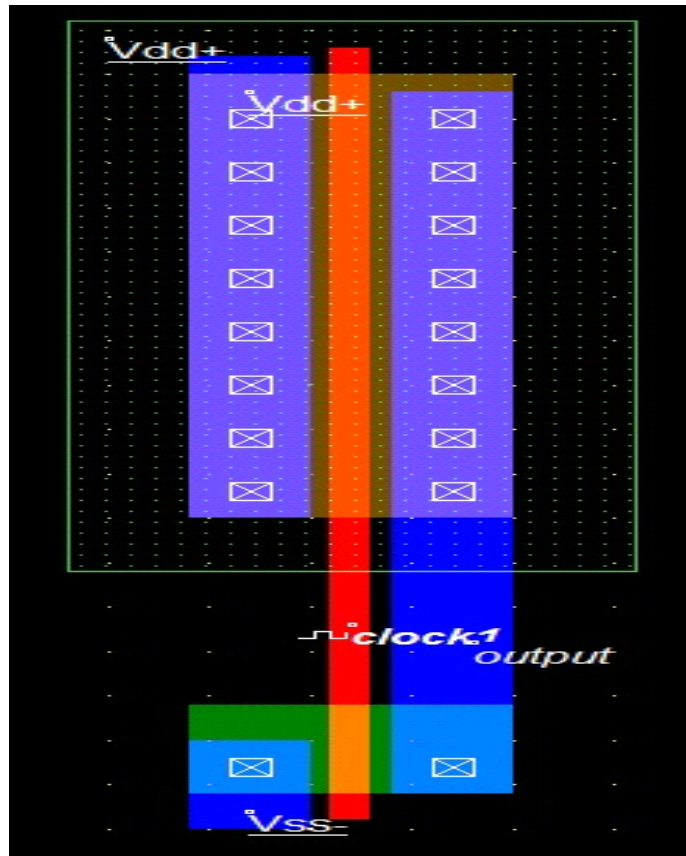
## **Design Layout & Timing Diagram of CMOS Inverter**





NAME OF THE STUDENT:

CLASS:

ROLL NUMBER:
  
## Part A: Design Layout & Timing Diagram of CMOS NAND Gate without capacitor





NAME OF THE STUDENT:

CLASS:

ROLL NUMBER:

 
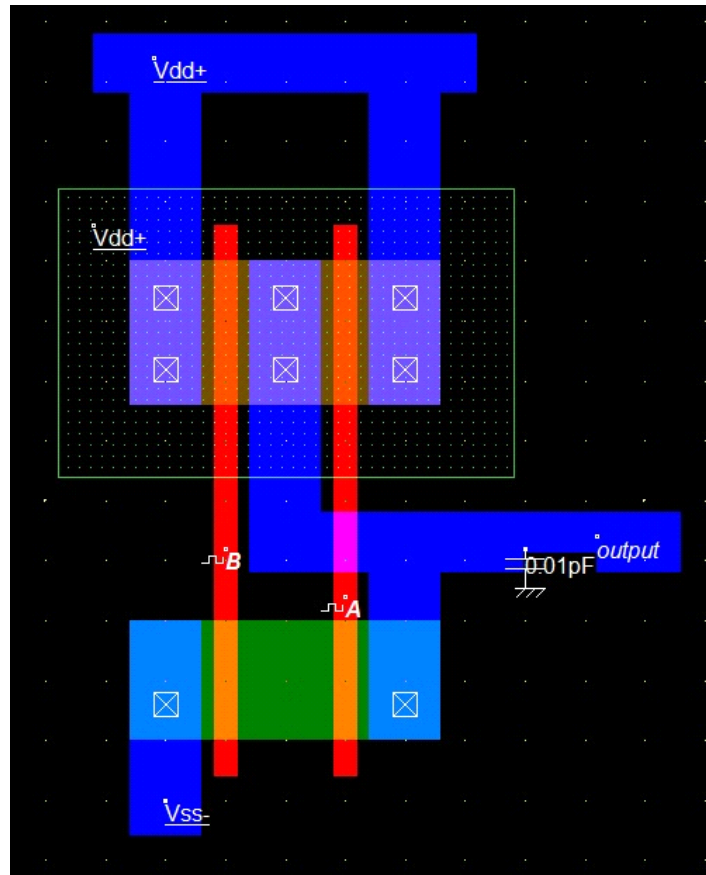
## Part B: Design Layout & Timing Diagram of CMOS NAND Gate with capacitor



NAME OF THE STUDENT:  
CLASS:  
ROLL NUMBER:


  
## Part A: Design Layout & Timing Diagram of CMOS NOR Gate without capacitor





NAME OF THE STUDENT:



CLASS:

ROLL NUMBER:
  
## Part B: Design Layout & Timing Diagram of CMOS NOR Gate with capacitor



  NAME OF THE STUDENT:  
CLASS:  
ROLL NUMBER:





NAME OF THE STUDENT:

CLASS:


ROLL NUMBER:



  


NAME OF THE STUDENT:  
 CLASS:  
 ROLL NUMBER:

**Layout Diagram:**

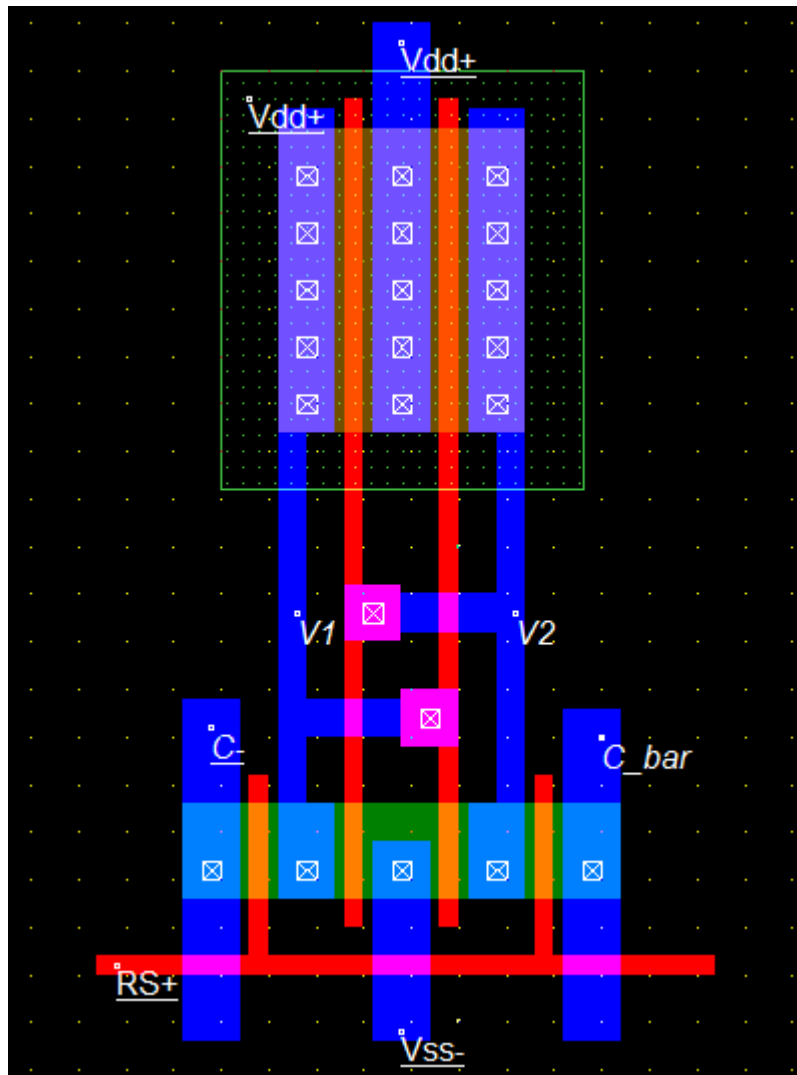

---

 NAME OF THE STUDENT:  
CLASS:  
ROLL NUMBER:



Display

- ☒ Delay
- ☒ Bus value between...

and...

v2

Evaluate

- ☐ Min/max/Av
- ☐ Frequency

v2

FFT

Time Scale

2 ns

Step (ps)

0.300



More

Reset

Print

Close

## Simulation Results:

 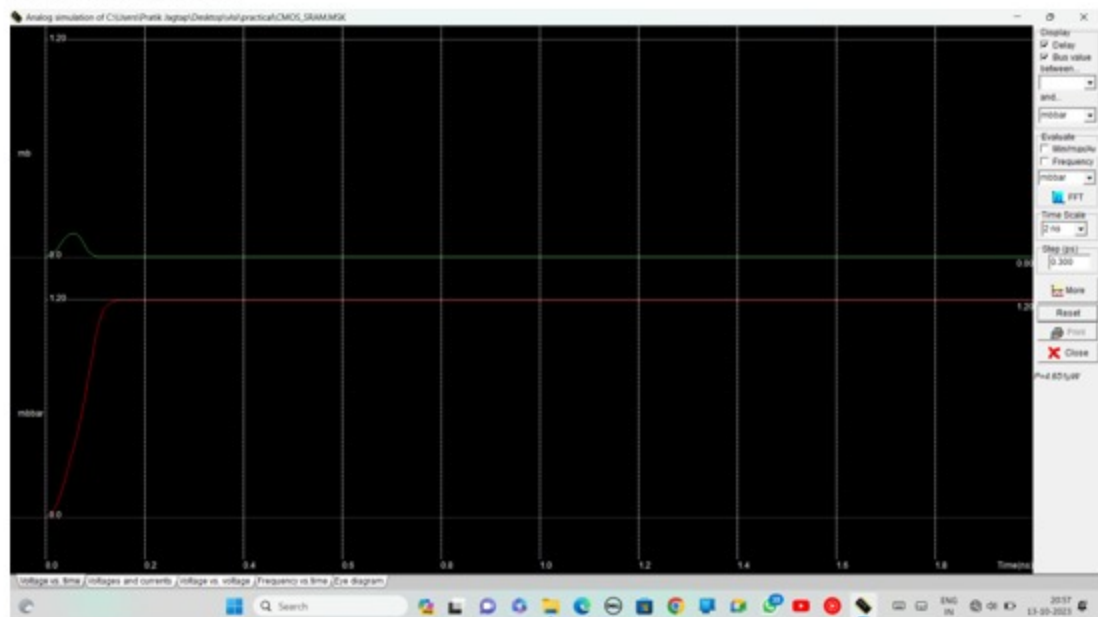

## Conclusion:

NAME OF THE STUDENT:

CLASS:

ROLL NUMBER: